



Bachelor in Computer Vision

## Digital Electronics Practice

Cedric Lemaitre  
c.lemaitre58@gmail.com

### ┌ Digital Electronic basics ┐

#### └ Problem 1 ┐

We consider an adder which allow to add 4 signals of 1 bit each.

- make the truth table
- obtain non-simplify equation
- make Karnaugh simplification
- make the schematic of the design using TTL component for :
  - non-simplify equation
  - simplification
- for each design made an estimation of processing time.